

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech. (Electronics & Electrical Engineering)(Sem.-4)

DIGITAL ELECTRONICS

Subject Code :BTEEE-401-18

M.Code :77574

Date of Examination : 02-07-22

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A

1. Write briefly :

- a. Discuss the need of digital system.
- b. What do you mean by tri-state logic? Discuss.
- c. How combinational circuits are different from sequential circuits? Explain.
- d. Discuss the significance of multiplexer.
- e. List the advantages of QM method.
- f. State DeMorgan's theorems.
- g. What do you mean by MOD of a counter? How many flip -flops are required for MOD-10 counter?
- h. What is the need of S/H circuit? Discuss.
- i. Write down the various characteristics of digital ICs.
- j. List the advantages of dual slope type A/D converter.

SECTION-B

2. Prove that NAND and NOR gates are universal gates.
3. Reduce the following expression to simplest Sum of product form using K-Map method $\Sigma m(2,3,5,7,10,13,14)$.
4. Draw the logic diagram and explain the working of a 4 bit synchronous counter.
5. In an industry four operations- Temperature, Pressure, Level and Humidity are to be encoded. Design a priority encoder in which Temperature must have the highest priority then Pressure followed by Level and Humidity is having the lowest priority.
6. Discuss the working of counter type A/D converter in detail.

SECTION-C

7. Discuss the working of :
 - a) R-2R D/A converter.
 - b) BCD adder.
8. Draw the logic diagrams and explain (in detail) the working of SR, JK, D and T flip-flops.
9. Explain Fan out, Fan in, Current and voltage parameters *w.r.t.* logic families. Discuss TTL and MOS logic families. Also, compare these logic families on the basis of propagation delay, noise immunity, Fan out, Fan in and power dissipation.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.