

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

**B.Tech.(ME) (Sem.-3)**  
**BASIC ELECTRONICS ENGINEERING**

Subject Code : BTEC305-18

M.Code : 76420

Date of Examination: 26-05-2023

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTIONS TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

**SECTION-A**

**1. Write Briefly :**

- a) What is peak inverse voltage?
- b) What is breakdown voltage?
- c) What are filter circuits?
- d) What is center tap full wave rectifier?
- e) What is meant by LSB and MSB.
- f) What is photo diode? Which material is used for them?
- g) What is operating point?
- h) What is comparator?
- i) What is the truth table of NAND and NOR gate?
- j) Convert the hexadecimal number into octal:
  - i. 5B.34
  - ii. 3DE

## SECTION-B

2. Explain the working of full wave rectifier with filtered output.
3. Draw and explain the three basic configurations of NPN transistor.
4. Explain with diagram how an op-amp can be used as phase shifter.
5. Explain JK flip flop with its truth table.
6. Solve the following :
  - a)  $(5735.20)_8 = (?)_2 = (?)_{16}$
  - b)  $(A152)_{16} = (?)_8 = (?)_2$
  - c) Add  $(100000.001)_2 = (11110.111)_2$

## SECTION-C

7. Explain the block diagram of an operational amplifier? Also draw the pin diagram of 741 op-amp.
8. Explain the working of an Emitter Follower and show how it performs the function of impedance transformation.
9. **Write short note on the following :**
  - a) SR Flip flop
  - b) Common mode rejection ratio and slew rate in op-amp

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**