

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech. (Electronics & Communication Engineering) (Sem.-4)

ANALOG CIRCUITS

Subject Code : BTEC-401-18

M.Code : 77565

Date of Examination : 20-11-2023

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A

1. Answer briefly :

- a) What do you mean by Avalanche effect and Zener effect?
- b) Define dynamic resistance of a PN junction diode in forward biasing.
- c) What is current series feedback?
- d) Classify the power amplifier based on the position of Q point on the ac load line.
- e) Why is the efficiency of class a amplifier is the lowest of all the power amplifiers?
- f) What is loop gain feedback amplifier?
- g) What are the uses of two transistors in Wein bridge oscillator?
- h) What is the difference between Class-B and class-AB operations?
- i) Compare AC amplifier and DC amplifier.
- j) Explain the importance of multistage amplifiers.

SECTION-B

2. Define Alpha and Beta of a transistor and derive the relationship between them.
3. Draw the circuit of transistor in common emitter configuration. Sketch the output characteristics. Indicate the active, saturation and cut-off regions.
4. What is Barkhausen criterion for oscillations?
5. Explain stabilization of gain with negative feedback.
6. Derive the expression for following parameters for a class B push-pull amplifier :
 - a) Q-point
 - b) DC input power
 - c) AC output power
 - d) Maximum Efficiency.

SECTION-C

7. Explain the working of Transformer coupled and Direct coupled amplifier with diagram.
8. For a transformer coupled class A amplifier, derive the expression for the following:
 - a) I_{CQ} and V_{CEQ}
 - b) AC output power P_{ac}
 - c) DC output power P_{dc}
 - d) % Efficiency
 - e) Maximum efficiency.
9. Write short note on the following :
 - a) Wein Bridge oscillator
 - b) Push pull amplifier.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.