

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

**B.Tech.(ME) Sem.-3)**  
**BASIC ELECTRONICS ENGINEERING**

Subject Code : BTEC305-18

M.Code : 76420

Date of Examination: 15-12-2023

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTIONS TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

**SECTION-A**

**1. Write briefly :**

- a) Define the functioning of rectifiers.
- b) What are the applications of zener diodes?
- c) Enlist various opto electronic devices.
- d) Draw the basic structure of BJT.
- e) What is the significance of operating point in BJTs?
- f) Draw the block diagram of Op-Amp.
- g) Describe the concept of virtual ground.
- h) What are the applications of Op-Amp?
- i) Write truth table of T and D flip flops.
- j) Draw NAND and XOR gates symbols.

### SECTION-B

2. Explain full wave rectifier with a suitable diagram.
3. Draw and explain nMOS.
4. Design square wave generator using Op-Amp.
5. Convert decimal number 55.5 into binary, octal and hexadecimal number systems.
6. What are the limitations of SR flip flop? How can we overcome these in JK flip flop?

### SECTION-C

7. Explain various breakdown mechanisms with neat and clean diagrams.
8. Design all three configurations of bipolar junction transistor.
9. Subtract 21 from 32 using 1's complement method.

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**